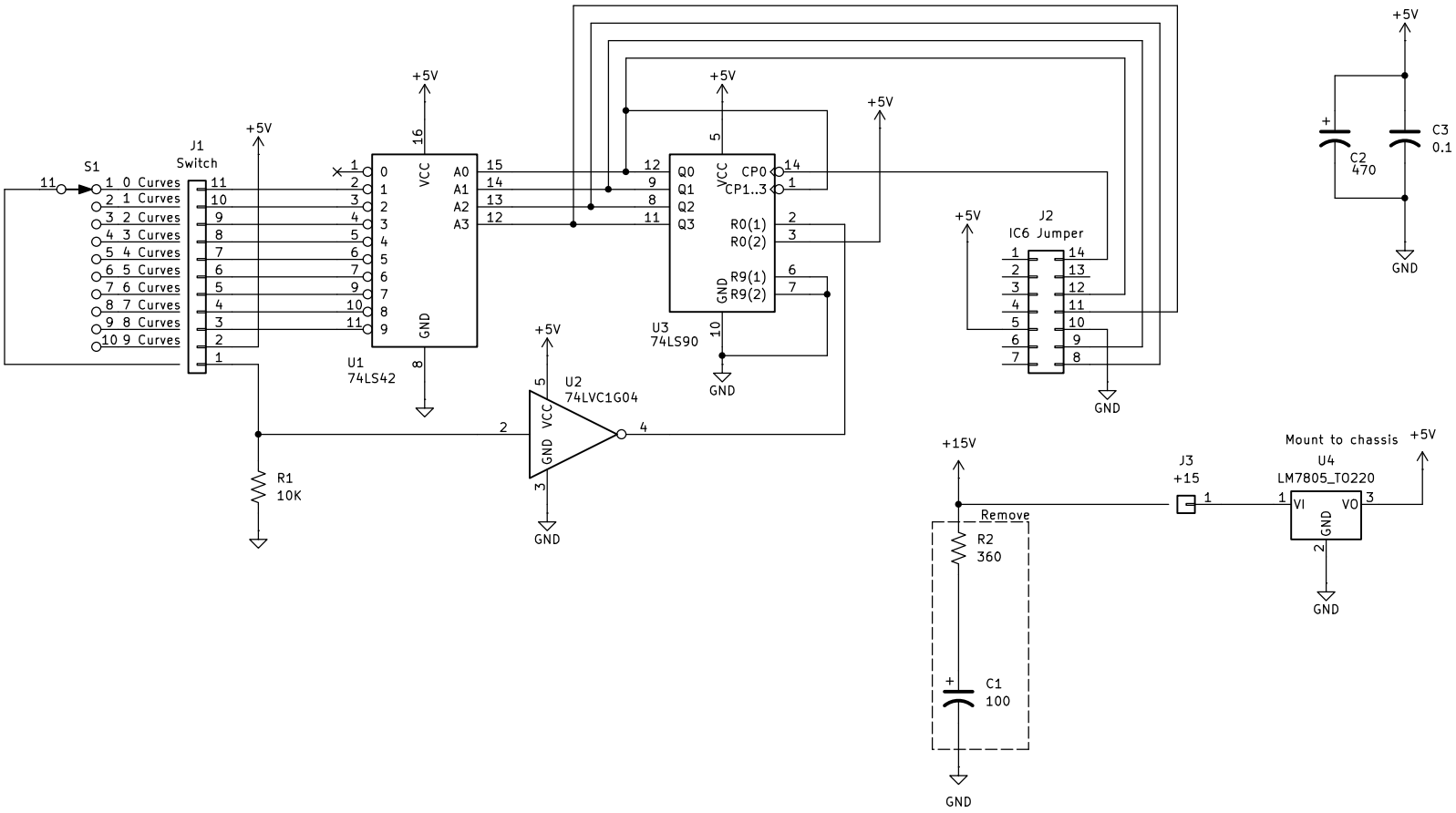



This circuit replaces the reset logic of the sweep generator by simply plugging into the 74LS90 socket on the PCB and adding a +15V supply pickoff to the main board. J1 is a 14-pin ribbon cable jumper to that socket. The sweep generator reset transistors and resistors should be removed, as well as the +5V dropping resistor and filter capacitor.

Enhancements:

1. The 7.5M potentiometer used in the original circuit is no longer available. This circuit changes from a current sense reset circuit to a digital BCD code reset. It uses a 10 position rotary switch to set the number of curves desired. The switch has positive detent stops which are more precise than fiddling with a potentiometer and offers repeatable and accurate setting.